



Kasarani Campus
Off Thika Road
Tel. 2042692 / 3
P. O. Box 49274, 00100
NAIROBI
Westlands Campus
Pamstech House
Woodvale Grove
Tel. 4442212
Fax: 4444175

KIRIRI WOMENS' UNIVERSITY OF SCIENCE AND TECHNOLOGY
UNIVERSITY EXAMINATION, 2022/2023 ACADEMIC YEAR
SECOND YEAR, FIRST SEMESTER EXAMINATION
FOR THE DEGREE OF BACHELOR OF SCIENCE
(COMPUTER SCIENCE)

Date: 26th July 2022
Time: 8.30am –10.30am

KCS 203 - ELECTRONICS

INSTRUCTIONS TO CANDIDATES

ANSWER QUESTION ONE (COMPULSORY) AND ANY OTHER TWO QUESTIONS

QUESTION ONE (30 MARKS)


- a) Differentiate between AC and DC current. (2 marks)
- b) Define the following terms as used in electrostatic. (2 marks)
- i) Electromotive force (emf)
 - ii) Electric Charge
 - iii) Resistance (2 marks)
- c) Three Resistors $R_1 = 2\Omega$, $R_2 = 4\Omega$ and $R_3 = 6\Omega$ are connected in parallel in a circuit with a 24V voltage source.
- i) Find the equivalent resistance (2 marks)
 - ii) Find the current across each resistor. (4 marks)
 - iii) What is the total current in the circuit? (4 marks)
- d) Briefly explain the two main types of semi-conductors (4 marks)
- e) Doping is the process of adding impurities to a pure semi-conductor. Why do we add impurities to a pure semi-conductor? (2 marks)
- f) Give three applications of each of the following types of diodes
- i) Zener diode (3 marks)
 - ii) Tunnel Diode (3 marks)

QUESTION TWO (20 MARKS)

- a) Define tunnel diode and briefly discuss tunnelling effect. (6 marks)
- b) What is depletion layer in a p-type and n-type semi-conductor. With the help of a diagram explain is formed. (8 marks)
- c) Explain the term doping. What is the effect of temperature on extrinsic semiconductor? (6 marks)

QUESTIONS THREE (20 MARKS)

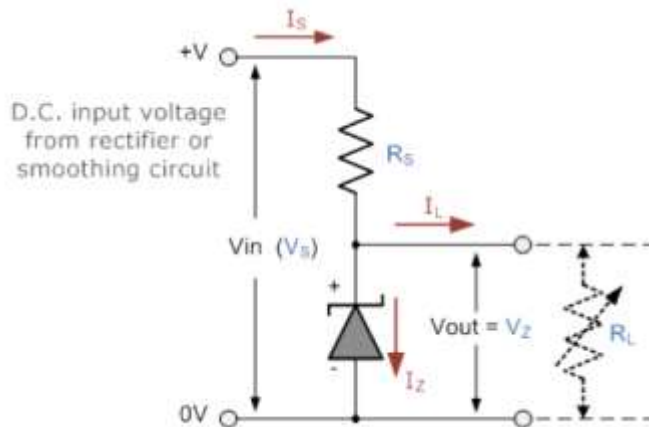- a) Discuss the differences between p-type and n-type semi-conductor materials? (8 marks)
- b) The figure below shows a zener regulator circuit.



A 5.0V stabilized power supply is required to be produced from a 12V DC power supply input source. The maximum power rating P_Z of the zener diode is 2W. Using the zener regulator circuit above calculate.

- i) The maximum current flowing through the zener diode. (3 marks)
- ii) The minimum value of the series resistor, R_S (3 marks)
- iii) The load current I_L if a load resistor of $1k\Omega$ is connected across the zener diode. (3 marks)
- iv) The zener current I_Z at full load. (3 marks)

QUESTION FOUR (20 MARKS)

- a) Explain the following zener diode specification
 - i) Zener voltage
 - ii) Current I_z (max)
 - iii) Current I_z (min)
 - iv) Power rating (8 marks)
- b) Differentiate between forward bias and reverse bias (4 marks)
- c) Briefly discuss the two types of Metal Oxide Semiconductor Field Effect Transistor (MOSFET) (4 marks)
- d) A transistor has a β_{DC} of 250 and a base current, I_B , of $10\mu A$. Calculate the collector current, I_C (4 marks)

QUESTION FIVE (20 MARKS)

- a) Define a transistor and briefly explain the transistor biasing? (4 marks)
- b) With the aid of a well labeled diagram, Discuss three configuration characteristics of a bipolar transistor. (12 marks)
- c) Explain the following operation modes in Bipolar Junction Transistor (BJT)
 - i) Cut-off mode
 - ii) Saturation mode (4 marks)