



Kasarani Campus  
Off Thika Road  
Tel. 2042692 / 3  
P. O. Box 49274, 00100  
NAIROBI  
Westlands Campus  
Pamstech House  
Woodvale Grove  
Tel. 4442212  
Fax: 4444175

**KIRIRI WOMENS' UNIVERSITY OF SCIENCE AND TECHNOLOGY**  
**UNIVERSITY EXAMINATION, 2022/2023 ACADEMIC YEAR**  
**SECOND YEAR, FIRST SEMESTER EXAMINATION**  
**FOR THE BACHELOR OF SCIENCE IN COMPUTER SCIENCE**  
**KCS 203- ELECTRONICS**

Date: 7<sup>th</sup> December, 2022  
Time: 8:30am – 10:30am

**INSTRUCTIONS TO CANDIDATES**

**ANSWER QUESTION ONE (COMPULSORY) AND ANY OTHER TWO QUESTIONS**

**QUESTION ONE (30 MARKS)**


- a) Define diode. (2 Marks)
- b) Briefly explain the following.
  - i) Doping
  - ii) Donor atom
  - iii) Acceptor atom (6 Marks)
- c) Define beta of a transistor. (2 Marks)
- d) A transistor has a  $\beta_{DC}$  of 250 and a base current,  $I_B$ , of  $20 \mu A$ . Calculate the collector current,  $I_C$ . (4 Marks)
- e) Define the following types of diodes.
  - i) Photo diode
  - ii) Zener diode
  - iii) Tunnel diode (6 Marks)
- f) Junction field effect transistor is a three-terminal semiconductor transistor, name the three terminals and explain the function of each terminal. (6 Marks)
- g) Briefly explain the difference between RC Coupled Amplifier and Direct Coupled Amplifier. (4 Marks)

**QUESTION TWO (20 MARKS)**

- a) Briefly Explain the following.
  - i) Tunneling Effect as used with tunnel diode (4 Marks)
  - ii) The working of photodiode (4 Marks)
- b) What is depletion layer in a p-type and n-type semi-conductor. With the help of a diagram explain how it is formed. (8 Marks)
- c) Explain the term doping. What is the effect of temperature on extrinsic semiconductor? (6 Marks)

### **QUESTIONS THREE (20 MARKS)**

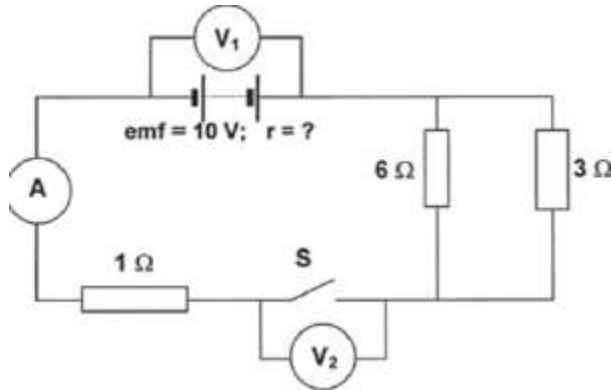- a) In the circuit represented below, the battery has an emf of 10 V and an unknown internal resistance. Voltmeter V<sub>1</sub> is connected across the battery and voltmeter V<sub>2</sub> is connected across the open switch S. The resistance of the connecting wires and ammeter can be ignored. Switch S is open.



- What is the reading on V<sub>1</sub>? (2 Marks)
  - What is the reading on V<sub>2</sub>? (2 Marks)
  - When Switch S is closed, the reading on V<sub>1</sub> drops to 7.5 V, what is the new reading on V<sub>2</sub>? (2 Marks)
  - Calculate the reading on the ammeter. (6 Marks)
  - Calculate the internal resistance of the battery. (4 Marks)
- b) Using a suitable example, show that two resistors connected in parallel will always have resulting total resistance less than the resistance of the individual resistors. (4 Marks)

### **QUESTION FOUR (20 MARKS)**

- a) Define transistor biasing, with the help of a diagram explain the difference between forward and reverse biasing. (8 Marks)
- b) Explain the following operation modes in Bipolar Junction Transistor (BJT) (4 Marks)
- Cut-off mode
  - Saturation mode
- c) You are provided with a 12V A.C. source, four diodes and a resistor.
- Draw a circuit diagram for full wave rectifier and show the points at which the output is taken. (4 Marks)
  - Sketch a graph of voltage against time before rectification. (2 Marks)
  - Sketch a voltage – time graph after rectification. (2 Marks)

### **QUESTION FIVE (20 MARKS)**

- a) Differentiate between NPN and PNP bipolar Junction Transistor? (4 Marks)
- b) With the aid of diagram, Explain the following configurations of Bipolar Junction Transistor.
- Common Base Configuration (4 Marks)
  - Common Emitter Configuration (4 Marks)
  - Common Collector Configuration (4 Marks)
- c) State the advantages of MOSFET over BJT in power electronics. (4 Marks)